

AN11996

QN908x Hardware Design Considerations

Rev. 1.3 — April 2018

Table 1. Document information

Info	Content
Keywords	QN908x, BLE, clock, power supply, PCB layout, DC-DC
Abstract	This application note describes the board design considerations for QN9080 and QN9083.



Table 2. Revision history

Rev	Date	Description
0.1	20160823	Initial version.
0.2	20160902	Updated the clock source name.
1.0	20170614	Public release.
1.1	20171110	Updated Table 9 .
1.2	20180102	Various small updates.
1.3	20180404	Updated Section 5.4.1, "Square wave" .

Contact information

For additional information, please visit: www.nxp.com

1. Introduction

QN908x is an ultra-low power, high-performance, and highly-integrated Bluetooth v5.0 Low Energy (BLE) solution for Bluetooth Smart applications. It integrates a BLE radio, controller, protocol stack, and profile software on a single chip, providing a flexible and easy-to-use BLE SoC solution. It also includes a high-performance MCU (32-bit ARM® Cortex®-M4F), on-chip memory, and peripherals to develop a truly single-chip wireless MCU solution.

2. System block diagram

The QN908x SoC includes the ARM Cortex-M4F core, the BLE 5.0 IP stack, and abundant peripherals.

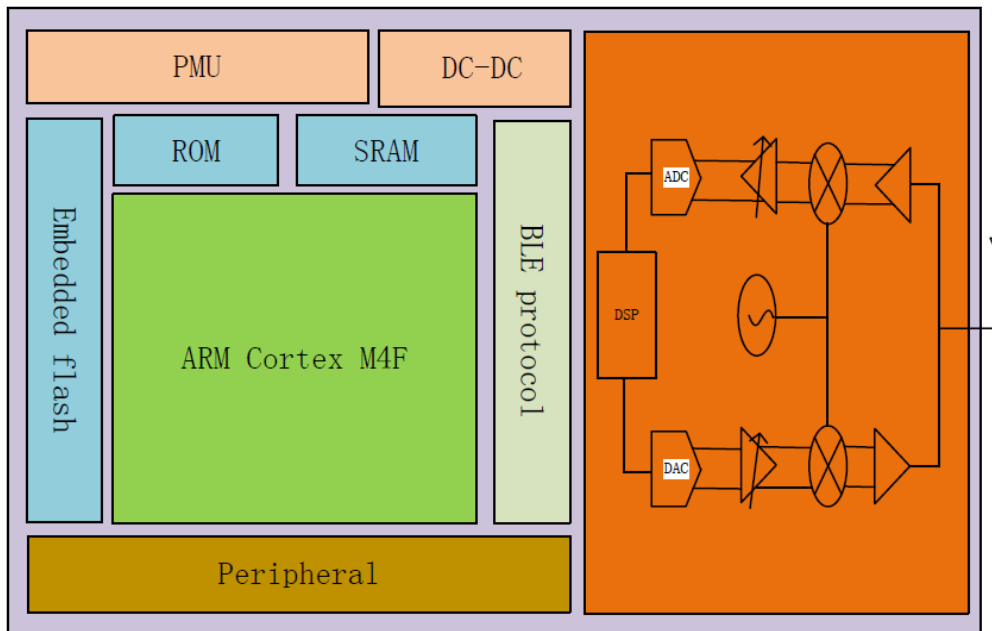


Fig 1. QN908x chip block diagram

3. Pin diagram and pin mux

QN908x offers two packages, while QN9080 has the HVQFN48 6x6 mm package and QN9083 has the WLCSP 3.2x3.2 mm package.

3.1 QN9080 HVQFN48 pin diagram

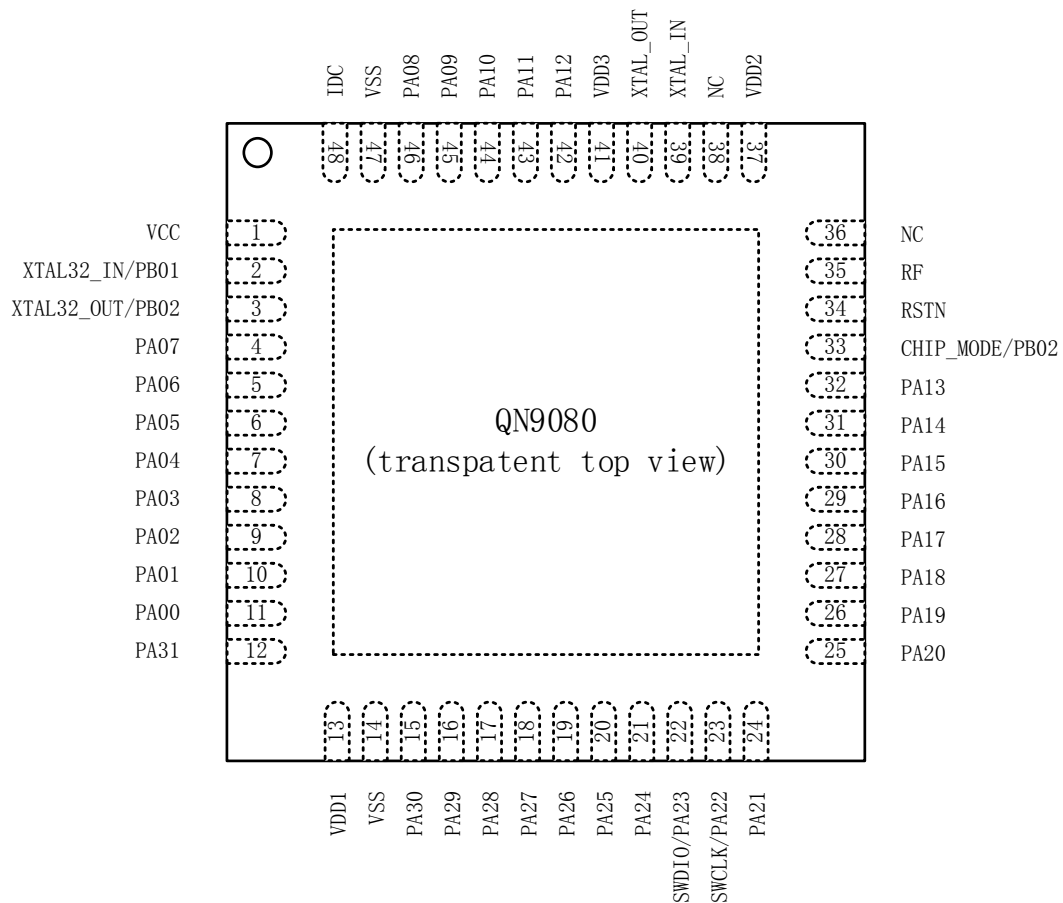


Fig 2. QN9080 pin diagram

3.2 QN9080 QFN48 pin mux

Table 3. QN9080 pin mux

PIN_CTRL	Name	FUNC0	FUNC1	FUNC2	FUNC3	FUNC4	FUNC5	FUNC6
[2-0]	PA00	GPIOA0 (I/O)	ADC0 (A)	PWM_OUT0 (O)	TIMO_CAPO (I)	FC0_RTS_SCL_SSEL1 (I/O)	FC2_SSEL3 (I/O)	WLAN_TX (I)
[5-3]	PA01	GPIOA1 (I/O)	ADC1 (A)	PWM_OUT1 (O)	TIMO_CAP1 (I)	FC0_CTS_SDA_SSEL0 (I/O)	FC2_SSEL2 (I/O)	WLAN_RX (I)
[8-6]	PA02	GPIOA2 (I/O)	QDEC0_A (I)	PWM_OUT2 (O)	TIMO_OUT0 (O)	CHRG_SDA (I/O)	FC2_RTS_SCL_SSEL1 (I/O)	RX_EN (O)
[11-9]	PA03	GPIOA3 (I/O)	QDEC0_B (I)	PWM_OUT3 (O)	TIMO_OUT1 (O)	CHRG_SCL (O)	FC2_CTS_SDA_SSEL0 (I/O)	TX_EN (O)
[14-12]	PA04	GPIOA4 (I/O)	ADC2 (A)	PWM_OUT4 (O)	TIMO_OUT0 (O)	FC0_TXD_SCL_MISO (I/O)	FC2_RXD_SDA_MOSI (I/O)	QSPI_DAT0 (I/O)
[17-15]	PA05	GPIOA5 (I/O)	ADC3 (A)	PWM_OUT5 (O)	TIMO_OUT1 (O)	FC0_RXD_SDA_MOSI (I/O)	FC2_TXD_SCL_MISO (I/O)	QSPI_DAT1 (I/O)
[20-18]	PA06	GPIOA6 (I/O)	VBG_EXCAP (A)	PWM_OUT3 (O)	TIMO_OUT2 (O)	FC1_RTS_SCL_SSEL1 (I/O)	BLE_PT10 (O)	QSPI_SCK (O)
[23-21]	PA07	GPIOA7 (I/O)	YREF_EXT (A)	PWM_OUT2 (O)	TIM1_CAPO (I)	FC1_CTS_SDA_SSEL0 (I/O)	BLE_PT11 (O)	QSPI_nCS (O)
[26-24]	PA08	GPIOA8 (I/O)	ADC4 (A)	PWM_IN0 (I)	TIM1_CAP1 (I)	FC1_TXD_SCL_MISO (I/O)	BLE_PT12 (O)	QSPI_DAT2 (I/O)
[29-27]	PA09	GPIOA9 (I/O)	ADC5 (A)	PWM_IN1 (I)	TIM1_OUT0 (O)	FC1_RXD_SDA_MOSI (I/O)	BLE_PT13 (O)	QSPI_DAT3 (I/O)
[32-30]	PA10	GPIOA10 (I/O)	ADC6 (A)	PWM_IN2 (I)	TIM1_OUT1 (O)	FC1_SCK (I/O)	ACMP0_OUT (O)	BLE_TX (O)
[35-33]	PA11	GPIOA11 (I/O)	ADC7 (A)	PWM_IN3 (I)	TIM1_OUT2 (O)	FC2_SSEL2 (I/O)	ACMP1_OUT (O)	BLE_RX (O)
[38-36]	PA12	GPIOA12 (I/O)	CHRG_SCL (O)	PWM_OUT5 (O)	ACMP0_OUT (O)	FC1_TXD_SCL_MISO (I/O)	DACO (O)	ANTENA (O)
[41-39]	PA13	GPIOA13 (I/O)	CHRG_SDA (I/O)	PWM_OUT4 (O)	ACMP1_OUT (O)	FC1_RXD_SDA_MOSI (I/O)	FC3_RTS_SCL_SSEL1 (I/O)	EXPA (O)
[44-42]	PA14	GPIOA14 (I/O)	CS0/ANA_TP0 (A)	ANTENA (O)	TIM2_CAPO (I)	FC0_RTS_SCL_SSEL1 (I/O)	FC3_CTS_SDA_SSEL0 (I/O)	QDEC1_A (I)
[47-45]	PA15	GPIOA15 (I/O)	CS1/ANA_TP1 (A)	PWM_OUT0 (O)	TIM2_CAP1 (I)	FC0_CTS_SDA_SSEL0 (I/O)	FC3_SCK (I/O)	QDEC1_B (I)
[50-48]	PA16	GPIOA16 (I/O)	CS2/ANA_TP2 (A)	PWM_OUT1 (O)	TIM2_OUT0 (O)	FC0_TXD_SCL_MISO (I/O)	FC3_RXD_SDA_MOSI (I/O)	QDEC0_A (I)
[53-51]	PA17	GPIOA17 (I/O)	CS3/ANA_TP3 (A)	DACO (O)	TIM2_OUT1 (O)	FC0_RXD_SDA_MOSI (I/O)	FC3_TXD_SCL_MISO (I/O)	QDEC0_B (I)
[56-54]	PA18	GPIOA18 (I/O)	CS4 (A)	PWM_OUT3 (O)	TIM2_OUT2 (O)	FC0_SCK (I/O)	FC3_SSEL2 (I/O)	BLE_SYNC (O)
[59-57]	PA19	GPIOA19 (I/O)	CS5 (A)	PWM_OUT2 (O)	EXPA (O)	FC0_SCK (I/O)	FC3_SSEL3 (I/O)	BLE_IN_PROC (O)
[62-60]	PA20	GPIOA20 (I/O)	QDEC1_A (I)	PWM_OUT1 (O)	TIM2_OUT0 (O)	SW0 (O)	FC1_RTS_SCL_SSEL1 (I/O)	QSPI_SCK (O)
[65-63]	PA21	GPIOA21 (I/O)	QDEC1_B (I)	PWM_OUT0 (O)	TIM2_OUT1 (O)	FC2_SSEL3 (I/O)	FC1_CTS_SDA_SSEL0 (I/O)	QSPI_nCS (O)
[68-66]	PA22	SWCLK (I)	GPIOA22 (I/O)	PWM_IN2 (I)	TIM3_OUT0 (O)	FC2_CTS_SDA_SSEL0 (I/O)	FC3_SSEL3 (I/O)	QDEC1_A (I)
[71-69]	PA23	SWDAT (I/O)	GPIOA23 (I/O)	PWM_IN3 (I)	TIM3_OUT1 (O)	FC2_RTS_SCL_SSEL1 (I/O)	FC3_SSEL2 (I/O)	QDEC1_B (I)
[74-72]	PA24	GPIOA24 (I/O)	ACMP0N/CS6 (A)	SWD_TRACEDAT0 (O)	TIM3_CAPO (I)	RX_EN (O)	FC3_RTS_SCL_SSEL1 (I/O)	QSPI_DAT0 (I/O)
[77-75]	PA25	GPIOA25 (I/O)	ACMP0P/CS7 (A)	SWD_TRACEDAT1 (O)	TIM3_CAP1 (I)	TX_EN (O)	FC3_CTS_SDA_SSEL0 (I/O)	QSPI_DAT1 (I/O)
[80-78]	PA26	GPIOA26 (I/O)	USB_DP (A)	PWM_IN0 (I)	TIM1_OUT0 (O)	FC2_RXD_SDA_MOSI (I/O)	QDEC0_A (I)	BLE_SYNC (O)
[83-81]	PA27	GPIOA27 (I/O)	USB_DM (A)	PWM_IN1 (I)	TIM1_OUT2 (O)	FC2_TXD_SCL_MISO (I/O)	QDEC0_B (I)	BLE_IN_PROC (O)
[86-84]	PA28	GPIOA28 (I/O)	CLK_AHB (O)	SWD_TRACECLK (O)	RTC_CAP (I)	FC1_SCK (I/O)	DACO (O)	QSPI_nCS (O)
[89-87]	PA29	GPIOA29 (I/O)	ACMP1N (A)	SWD_TRACEDAT2 (O)	TIM3_OUT0 (O)	FC2_SCK (I/O)	FC3_TXD_SCL_MISO (I/O)	QSPI_DAT2 (I/O)
[92-90]	PA30	GPIOA30 (I/O)	ACMP1P (A)	SWD_TRACEDAT3 (O)	TIM3_OUT1 (O)	FC2_SCK (I/O)	FC3_RXD_SDA_MOSI (I/O)	QSPI_DAT3 (I/O)
[95-93]	PA31	GPIOA31 (I/O)	DAC (A)	RTC_CAP (I)	TIM3_OUT2 (O)	SW0 (O)	FC3_SCK (I/O)	QSPI_SCK (O)
	PB00	GPIOB0 (I/O)	XTAL32_OUT					
	PB01	GPIOB1 (I/O)	XTAL32_IN					
	BOOT_mode	GPIOB2 (I/O)	ANTENA (O)					

3.3 QN9083 WLCSP pin diagram

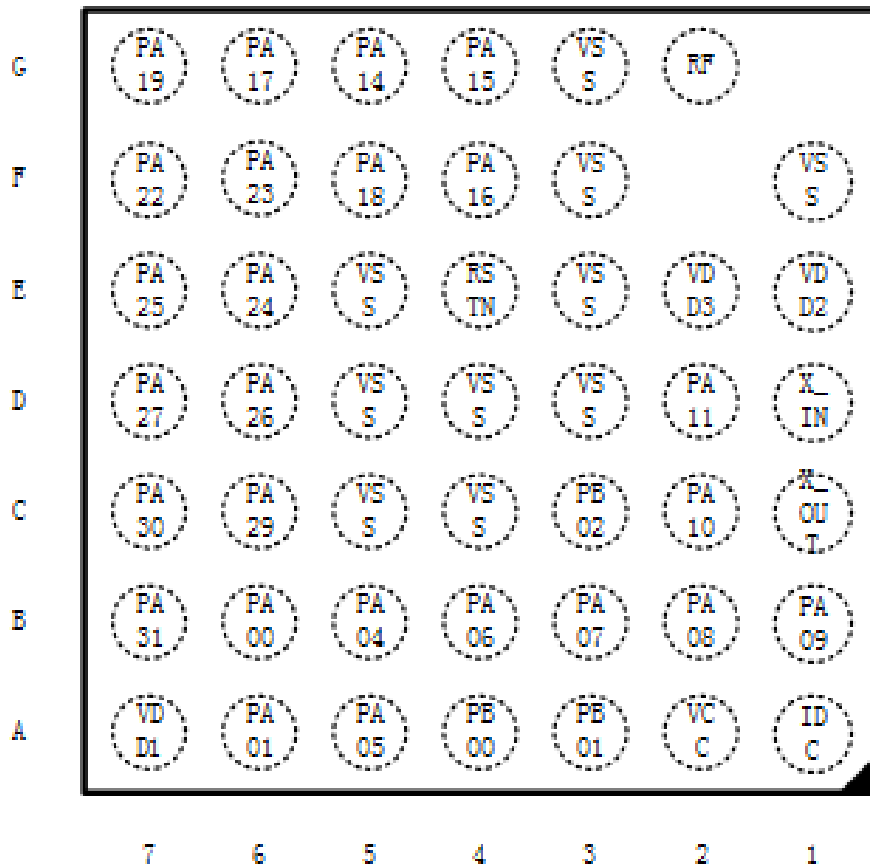


Fig 3. QN9083 pin diagram

3.4 QN9083 WLCSP pin mux

Table 4. QN9083 pin mux

PIN_CTRL	Name	FUNC0	FUNC1	FUNC2	FUNC3	FUNC4	FUNC5	FUNC6
[2-0]	PA00	GPIOA0 (I/O)	ADC0 (A)	PWM_OUT0 (O)	TIM0_CAP0 (I)	FC0_RTS_SCL_SSEL1 (I/O)	FC2_SSEL3 (I/O)	WLAN_TX (I)
[5-3]	PA01	GPIOA1 (I/O)	ADC1 (A)	PWM_OUT1 (O)	TIM0_CAP1 (I)	FC0_CTS_SDA_SSEL0 (I/O)	FC2_SSEL2 (I/O)	WLAN_RX (I)
[14-12]	PA04	GPIOA4 (I/O)	ADC2 (A)	PWM_OUT4 (O)	TIM0_OUT0 (O)	FC0_TXD_SCL_MISO (I/O)	FC2_RXD_SDA_MOSI (I/O)	QSPI_DAT0 (I/O)
[17-15]	PA05	GPIOA5 (I/O)	ADC3 (A)	PWM_OUT5 (O)	TIM0_OUT1 (O)	FC0_RXD_SDA_MOSI (I/O)	FC2_TXD_SCL_MISO (I/O)	QSPI_DAT1 (I/O)
[20-18]	PA06	GPIOA6 (I/O)	YBG_EXCAP (A)	PWM_OUT3 (O)	TIM0_OUT2 (O)	FC1_RTS_SCL_SSEL1 (I/O)	BLE_PT10 (O)	QSPI_SCK (O)
[23-21]	PA07	GPIOA7 (I/O)	VREF_EXT (A)	PWM_OUT2 (O)	TIM1_CAP0 (I)	FC1_CTS_SDA_SSEL0 (I/O)	BLE_PT11 (O)	QSPI_nCS (O)
[26-24]	PA08	GPIOA8 (I/O)	ADC4 (A)	PWM_IN0 (I)	TIM1_CAP1 (I)	FC1_TXD_SCL_MISO (I/O)	BLE_PT12 (O)	QSPI_DAT2 (I/O)
[29-27]	PA09	GPIOA9 (I/O)	ADC5 (A)	PWM_IN1 (I)	TIM1_OUT0 (O)	FC1_RXD_SDA_MOSI (I/O)	BLE_PT13 (O)	QSPI_DAT3 (I/O)
[32-30]	PA10	GPIOA10 (I/O)	ADC6 (A)	PWM_IN2 (I)	TIM1_OUT1 (O)	FC1_SCK (I/O)	ACMP0_OUT (O)	BLE_TX (O)
[35-33]	PA11	GPIOA11 (I/O)	ADC7 (A)	PWM_IN3 (I)	TIM1_OUT2 (O)	FC2_SSEL2 (I/O)	ACMP1_OUT (O)	BLE_RX (O)
[44-42]	PA14	GPIOA14 (I/O)	CS0/ANA_TP0 (A)	ANTENA (O)	TIM2_CAP0 (I)	FC0_RTS_SCL_SSEL1 (I/O)	FC3_CTS_SDA_SSEL0 (I/O)	QDEC1_A (I)
[47-45]	PA15	GPIOA15 (I/O)	CS1/ANA_TP1 (A)	PWM_OUT0 (O)	TIM2_CAP1 (I)	FC0_CTS_SDA_SSEL0 (I/O)	FC3_SCK (I/O)	QDEC1_B (I)
[50-48]	PA16	GPIOA16 (I/O)	CS2/ANA_TP2 (A)	PWM_OUT1 (O)	TIM2_OUT0 (O)	FC0_TXD_SCL_MISO (I/O)	FC3_RXD_SDA_MOSI (I/O)	QDEC0_A (I)
[53-51]	PA17	GPIOA17 (I/O)	CS3/ANA_TP3 (A)	DACO (O)	TIM2_OUT1 (O)	FC0_RXD_SDA_MOSI (I/O)	FC3_TXD_SCL_MISO (I/O)	QDEC0_B (I)
[56-54]	PA18	GPIOA18 (I/O)	CS4 (A)	PWM_OUT3 (O)	TIM2_OUT2 (O)	FC0_SCK (I/O)	FC3_SSEL2 (I/O)	BLE_SYNC (O)
[59-57]	PA19	GPIOA19 (I/O)	CS5 (A)	PWM_OUT2 (O)	EXPA (O)	FC0_SCK (I/O)	FC3_SSEL3 (I/O)	BLE_IN_PROC (O)
[68-66]	PA22	SWCLK (I)	GPIOA22 (I/O)	PWM_IN2 (I)	TIM3_OUT0 (O)	FC2_CTS_SDA_SSEL0 (I/O)	FC3_SSEL3 (I/O)	QDEC1_A (I)
[71-69]	PA23	SWDAT (I/O)	GPIOA23 (I/O)	PWM_IN3 (I)	TIM3_OUT1 (O)	FC2_RTS_SCL_SSEL1 (I/O)	FC3_SSEL2 (I/O)	QDEC1_B (I)
[74-72]	PA24	GPIOA24 (I/O)	ACMP0N/CS6 (A)	SWD_TRACEDAT0 (O)	TIM3_CAP0 (I)	RX_EN (O)	FC3_RTS_SCL_SSEL1 (I/O)	QSPI_DAT0 (I/O)
[77-75]	PA25	GPIOA25 (I/O)	ACMP0P/CS7 (A)	SWD_TRACEDAT1 (O)	TIM3_CAP1 (I)	TX_EN (O)	FC3_CTS_SDA_SSEL0 (I/O)	QSPI_DAT1 (I/O)
[80-78]	PA26	GPIOA26 (I/O)	USB_DP (A)	PWM_IN0 (I)	TIM1_OUT0 (O)	FC2_RXD_SDA_MOSI (I/O)	QDEC0_A (I)	BLE_SYNC (O)
[83-81]	PA27	GPIOA27 (I/O)	USB_DM (A)	PWM_IN1 (I)	TIM1_OUT2 (O)	FC2_TXD_SCL_MISO (I/O)	QDEC0_B (I)	BLE_IN_PROC (O)
[89-87]	PA29	GPIOA29 (I/O)	ACMP1N (A)	SWD_TRACEDAT2 (O)	TIM3_OUT0 (O)	FC2_SCK (I/O)	FC3_TXD_SCL_MISO (I/O)	QSPI_DAT2 (I/O)
[92-90]	PA30	GPIOA30 (I/O)	ACMP1P (A)	SWD_TRACEDAT3 (O)	TIM3_OUT1 (O)	FC2_SCK (I/O)	FC3_RXD_SDA_MOSI (I/O)	QSPI_DAT3 (I/O)
[95-93]	PA31	GPIOA31 (I/O)	DAC (A)	RTC_CAP (I)	TIM3_OUT2 (O)	SW0 (O)	FC3_SCK (I/O)	QSPI_SCK (O)
	PB00	GPIOB0 (I/O)	XTAL32_OUT					
	PB01	GPIOB1 (I/O)	XTAL32_IN					
	BOOT_mode	GPIOB2 (I/O)	ANTENA (O)					

4. Chip power supply

4.1 Power supply pins description

QN908x has four pins for the power supply input.

Table 5. Power descriptions

Pin name	Description
VCC	Chip power supply for the PMU (power management unit) and IOs
VDD1	Chip power supply for the digital core
VDD2	Chip power supply for the RF blocks
VDD3	Chip power supply for the analog blocks

For the power supply,

- **VCC** is the basic power supply for the PMU and the IOs. Its voltage can range from 1.8 V to 3.6 V.
- **VDD1** is the power supply for the internal core and digital blocks. Its voltage can range from 1.3 V to 3.6 V.
- **VDD2** is the power supply for the internal RF blocks. Its voltage can range from 1.3 V to 3.6 V.
- **VDD3** is the power supply for the internal analog blocks. Its voltage can range from 1.3 V to 3.6 V.

To improve power stability, the VCC pin should have a 4.7- μ F capacitor connected in parallel with a 0.1- μ F capacitor. The VDD1, VDD2, and VDD3 pins should have a 0.1- μ F capacitor connected.

4.2 Integrated DC-DC

To reduce power consumption, QN908x has an integrated DC-DC block, which can transform the voltage from VCC to 1.3 V and supply it to VDD1, VDD2, and VDD3. The DC-DC block outputs at the IDC pin and needs a 10- μ H inductor together with a 10-nH inductor in series, as well as a 1- μ F capacitor.

To disable the DC-DC function easily, there is an integrated switch which can connect VCC to IDC directly and is controlled by a software register.

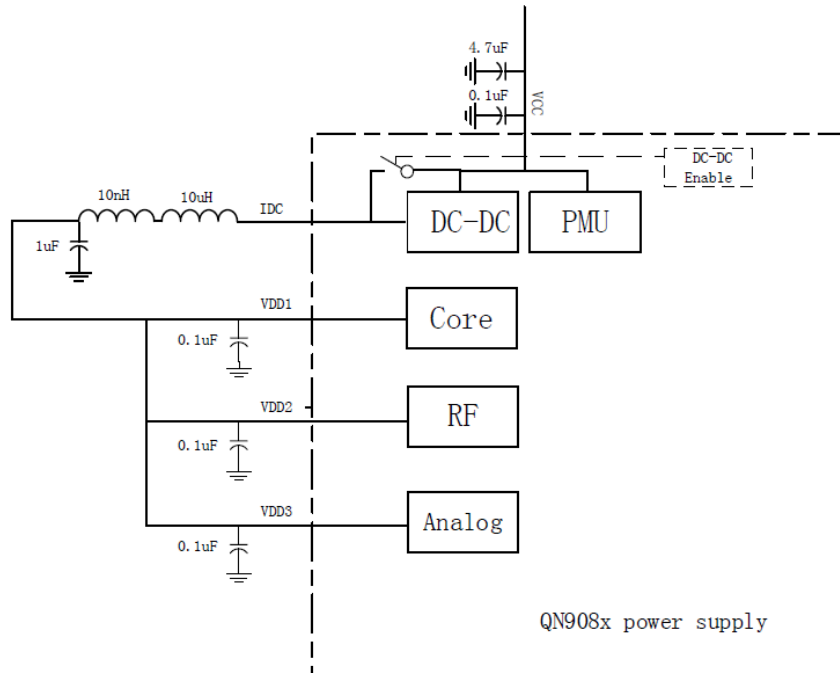


Fig 4. Power supply with an integrated DC-DC converter

If you decide to save the inductors by disabling the internal DC-DC, the VDD1, VDD2, and VDD3 can connect to VCC directly and the IDC pin should be floating.

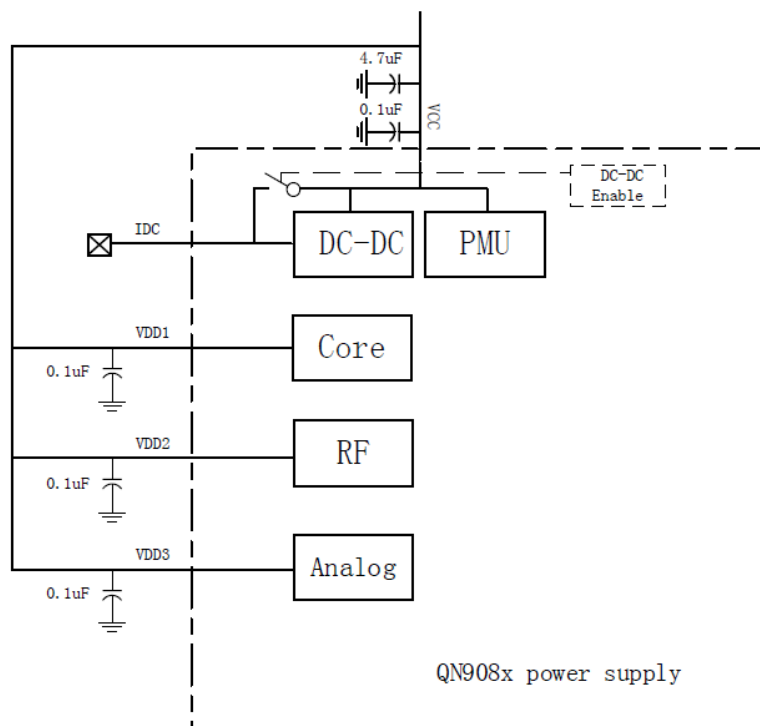


Fig 5. Power supply without an integrated DC-DC converter

4.3 DC-DC circuit

The DC-DC circuit needs external inductors and an output capacitor. Both the inductors and the output capacitor should be low-ESR. The inductors and the capacitor affect the DC-DC oscillating frequency. A 10- μ H inductor and a 1- μ F output capacitor result in a better efficiency of the DC-DC.

The inductor's actual value may change with the current, especially when the current starts to saturate the inductor with magnetic. Select an inductor with a sufficient current limitation. [Table 6](#) lists the verified components and their part numbers.

Table 6. Verified DC-DC inductor part number

Vendor	Part number	Inductor value
Murata	LQH2MCN100M52L	10 μ H
Murata	LQM21FN100M70L	10 μ H
TDK	MLZ2012M100W	10 μ H

5. Clock

QN908x needs two clocks to run. The high-frequency clock serves the MCU and peripherals. The BLE block and IP clocks are derived from the high-frequency clock. The low-frequency clock is the sleep clock which is used as the RTC timer source during the MCU power-down period.

5.1 16/32-MHz crystal oscillator (XTAL) and 32-MHz freely running oscillator (OSC32M)

There are two high-frequency sources available for QN908x. The first one is the external crystal (called XTAL) and the second is derived from the internal RC oscillator (called OSC32M). XTAL accepts only 16-MHz and 32-MHz crystals. QN908x integrates the load capacitor inside. Its adjusting range is 5 pF ~ 27.05 pF with a 0.33-pF pre-step. This integrated capacitor is controlled by a 6-bit register. If you enable the extra addition load capacitor option, the load capacitor adjusting range is 10 pF ~ 32.05 pF. The equivalent capacitor adjusting range is 2.5 pF ~ 13.525 pF and 5 pF ~ 16.025 pF.

Table 7. XTAL integrated load capacitors' parameters

Extra addition capacitor option	Capacitor range for the crystal	Capacitor pre-step for each	Equivalent load capacitor
NO	5 pF ~ 27.05 pF	0.33 pF	2.5 pF ~ 13.525 pF
YES	10 pF ~ 32.05 pF	0.33 pF	5 pF ~ 16.025 pF

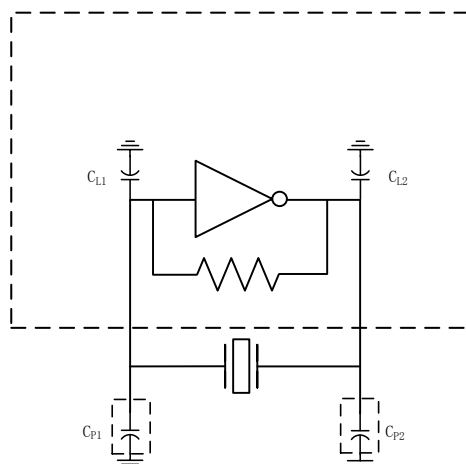


Fig 6. Crystal oscillator block

The load capacitors affect the frequency of the crystal oscillator.

In [Fig 6](#), C_{L1} and C_{L2} are the integrated load capacitors. C_{P1} and C_{P2} are the parasitic capacitors which form the packages' pads and the PCB layout.

$$\text{Equivalent load capacitor} = \frac{(C_{L1} + C_{P1}) \times (C_{L2} + C_{P2})}{C_{L1} + C_{P1} + C_{L2} + C_{P2}}$$

Assuming that $C_{L1} = C_{L2}$ and $C_{P1} = C_{P2}$, the equivalent load capacitor is $\frac{C_L}{2} + \frac{C_P}{2}$.

Choosing a crystal with a lower-load capacitor results in lower current consumption and shorter startup time. The suggested crystal parameters are shown in [Table 8](#).

Table 8. XTAL parameter

Crystal frequency	ESR	Load capacitor	Tolerance
32 MHz	<100 Ω	<= 10 pF	<= 20 ppm
16 MHz	<200 Ω	<= 10 pF	<= 20 ppm

Table 9. Verified XTAL part number

Vendor	Part number	Frequency	Accuracy	Load cap
MURATA	XRCGB32M000F2N13R0	32 MHz	10 PPM	8 pF
YOKE	S2016A-032000-T08-BDD-YNA	32 MHz	10 PPM	8 pF

5.2 32.768-kHz crystal oscillator (XTAL32K)

There are two low-frequency sources available for QN908x. The first is the external crystal (called XTAL32K). XTAL32K generates the clock using the external crystal with a frequency of 32.768 kHz. QN908x has also integrated load capacitors for XTAL32K and they are controlled by a 6-bit register. The load capacitors affect the frequency of XTAL32K.

The range of the adjustable load capacitors is shown in [Table 10](#).

Table 10. XTAL32K integrated load capacitors parameters

Extra addition capacitor option	Capacitor for the crystal	Capacitor pre-step for each	Equivalent load capacitor
NO	5 pF ~ 27.05 pF	0.4 pF	2.5 pF ~ 13.525 pF
YES	10 pF ~ 32.05 pF	0.4 pF	5 pF ~ 16.025 pF

The tolerance of the XTAL32K crystal affects the window size of the receiver, which impacts the power consumption.


The suggested XTAL32K crystal parameters are shown in [Table 11](#).

Table 11. XTAL32K parameters

Crystal frequency	ESR	Load capacitor	Tolerance
32.768 kHz	< 100 k Ω	<= 13 pF	<= 50 ppm

Table 12. Verified XTAL32K part number

Vendor	Part number	Frequency	Accuracy	Load cap
EPSON	FC-12M	32.768 kHz	20 ppm	12.5 pF

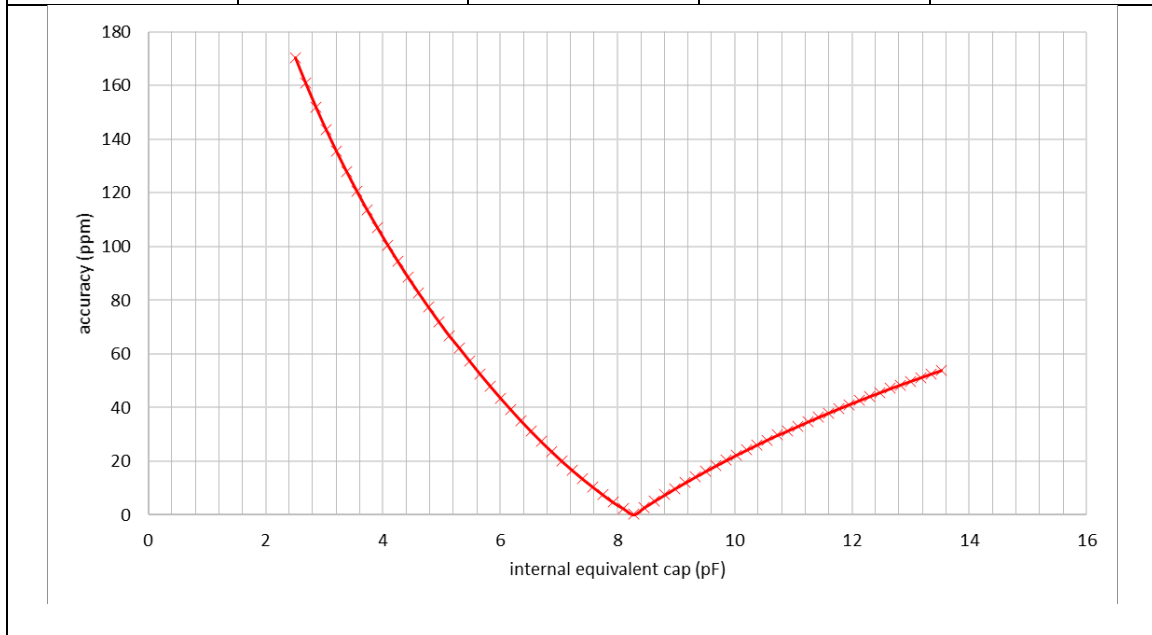

5.3 32-kHz freely running oscillator (RCO32K)

RCO32K is another clock source for the low-frequency clock. RCO32K uses the internal RC oscillator circuit to generate the clock. The frequency of RCO32K is 32 kHz. To keep the RCO32K frequency around 32 kHz, calibration is enabled when the chip powers up. To calibrate the clock, the software correcting process is started. After the calibration and compensation, the tolerance of the Sleep Timer and RTC is lower than 500 ppm.

RCO can also perform hardware calibration when the chip powers up and sets the clock close to 32 kHz. The chip is designed with a 22-bit counter to correct little deviations and make the RCO running around 32 kHz. Normally, RCO can offer a clock with a jitter of 150 ppm. In a long term, the RCO frequency drifts due to the temperature, voltage, and noise. It is necessary to perform the software calibration periodically to keep the Sleep Timer and RTC running in the range of 500 ppm.

Considering the temperature as the only factor, the RCO has the change rate of 160 ppm/°C.

5.4 Clock injection

Besides the internal oscillator, QN908x can also get the clock source using clock injection. For the high-frequency clock, the acceptable injection clock frequencies are 16 MHz and 32 MHz. Either a square wave or a sine wave can be injected to the chip. For the low-frequency clock, the chip accepts the 32.768-kHz clock in a square wave or a sine wave.

5.4.1 Square wave

If using the square-wave clock injection, the register of the clock source selection must be set for the square-wave clock injection.

A 1 nF cap should be added to the XTAL_IN signal if using a square wave.

With the square-wave clock, QN908x treats it as a digital signal and the clock must be injected from the XTAL_IN pin of QN908x, while the XTAL_OUT pin must be floating.

The square-wave clock must have a peak-to-peak voltage range from 2.5 V to VCC.

For a high frequency, the clock must be 16 MHz or 32 MHz.

For a low frequency, the clock must be 32.768 kHz.

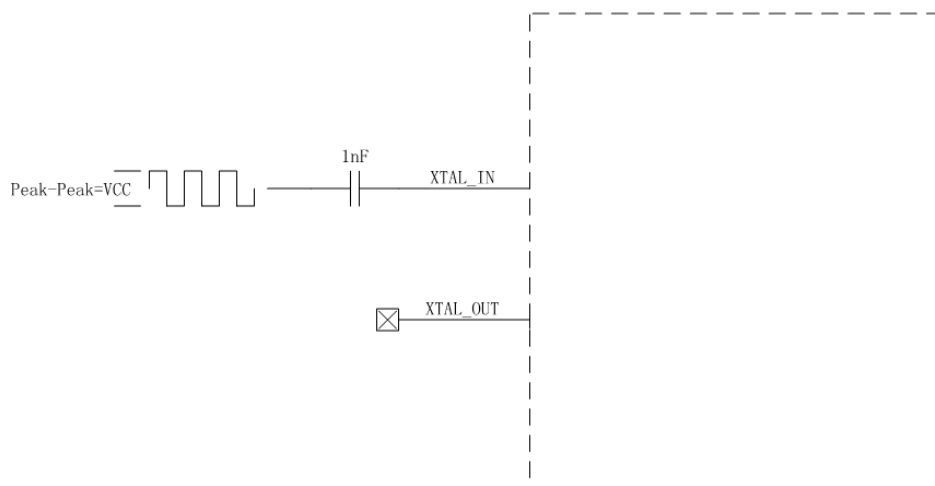


Fig 7. Square wave clock injection

5.4.2 Sine wave

If using the sine-wave clock injection, the register of the clock source selection must be set to the sine-wave clock injection and the QN908x treats it as an analog signal. While injecting the sine wave to the clock, a 1-nF capacitor must be used for AC coupling. The XTAL_OUT pin must connect to the GND with an AC coupling capacitor.

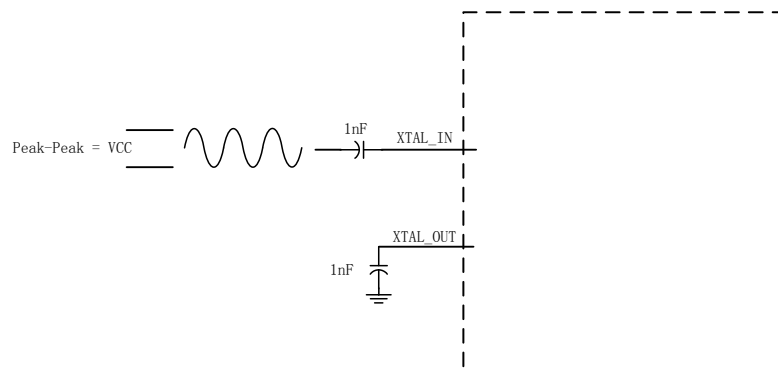


Fig 8. Sine wave clock injection

The voltage of the sine wave must have the peak to peak equal to the voltage of MIN {2.5 V, VCC}.

The high-frequency clock must be either 16 MHz or 32 MHz.

The low-frequency clock must be 32.768 kHz.

5.5 Clock output

QN908x supports the feature of outputting the XTAL and XTAL32K to the IO pins directly with the buffer and divider.

XTAL outputs at pins PA05, PA11, PA19, and PA25. XTAL32K outputs at pins PA04, PA10, PA18, and PA24. The GPIO pins and the divider are configurable using registers.

6. IOs

QN908x has a total of 35 IOs in the HVQFN package and 28 IOs in the WLCSP package.

The PB00 and PB01 of both the HVQFN package and the WLCSP package are the clock input pins of the XTAL32K by default.

The PB02 of both the HVQFN and WLCSP packages works in the CHIP_MODE function by default.

PA00 ~ PA31 are general IOs with seven alternate functions. By default, all general IOs are defined as GPIOs except for the SWDIO and SWCLK pins.

All QN908x's IOs have integrated pull-up and pull-down resistors, the IOs can be configured as pull-up, pull-down, or high-Z.

6.1 Pull-up and pull-down resistors

All GPIOs are set to the input function with the pull-up enabled by default after the powerup or reset. The integrated pull-up resistors have a value of roughly 100 k Ω and the pull-down resistors have a value of roughly 200 k Ω .

The pull-up and pull-down resistors values may change a bit with different VCC voltages.

6.2 IOs drive strength

There are four levels of drive strength supported by the GPIOs. An ordinary pin has the first two levels of drive strength, while PA6, PA11, PA19, PA26, and PA27 have four levels of drive strength. See [Table 13](#) for details.

Table 13. IOs drive strength

DRV_EXTRA	DRV_CTRL[X]	Source Current [mA]	Sink Current [mA]
0	0	1.4	0.8
0	1	5.5	3.1
1	0	13.8	—
1	1	17.9	—

6.2.1 Normal drive ability

The normal drive ability setting lets the IO to have roughly 3.5 mA of the source current and 2.5 mA of the sink current.

6.2.2 High drive ability

The high drive ability setting lets the IO to have roughly 13 mA of the source current and 7 mA of the sink current.

6.2.3 Extra-high drive ability

Five of the IOs have the extra-high source current setting.

PA06, PA11, PA19, PA26, and PA27 have extra-high source current. With the extra-high drive ability setting, these five IOs add an extra 26 mA of source current.

7. Debug and program

7.1 Debug port

7.1.1 SWD

QN908x supports the SWD debugging port which uses the GPIO PA22 as the SWDCLK and the GPIO PA23 as the SWDIO. The two pins should be configured as the SWD functions. Not sharing them with other functions is recommended for the system design.

7.1.2 ETM

QN908x has an integrated ETM (Embedded Trace Macro cell) interface, which enables the capturing of instructions while the MCU is running.

The ETM signals are at pins PA24, PA25, PA28, PA29, and PA30. However, PA28 is not available in the WLCSP package, so the ETM function is only supported in the HVQFN package.

7.2 Programing port

7.2.1 ISP

QN908x supports the ISP function via the Flexcomm0 UART, Flexcomm3 SPI, or USB interface. The pads are from PA14 to PA17 when using the UART/SPI for ISP. To enable the ISP mode, pull down the CHIP_MODE pin while the chip is reset. The chip is always in the ISP mode until the CHIP_MODE pin is pulled high. The ISP

function starts when a valid handshake is received, and it starts to receive the binary file and program the flash with a new binary file.

The CHIP_MODE pin is pull-up-enabled by default. It is recommended to keep it floating when the ISP process is finished to avoid the IO current leakage.

8. RF

QN908x has a 2.4-GHz RF port which is shared by the receiver and the transmitter. The RF port is designed with a 50-Ω impedance and the RF trace impedance connected to the Radio should be 50 Ω.

8.1 Harmonic rejection

The RF port can have some RF leakage at the harmonic frequency and may cause failure when passing certifications. Even the harmonic signal is rejected by the antenna that only has the resonance frequency of roughly 2.4 GHz (the carrier frequency). However, to make sure that the harmonic signal does not transmit to the open space, it is suggested to have a Pi circuit in front of the RF port which works as the filter to reject the undesired RF leakage.

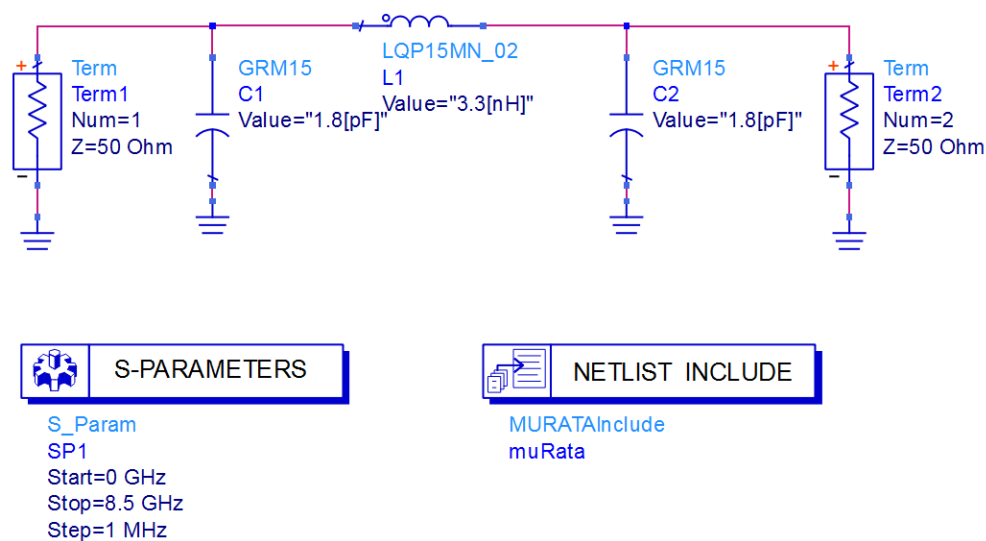


Fig 9. Harmonic frequency rejection filter

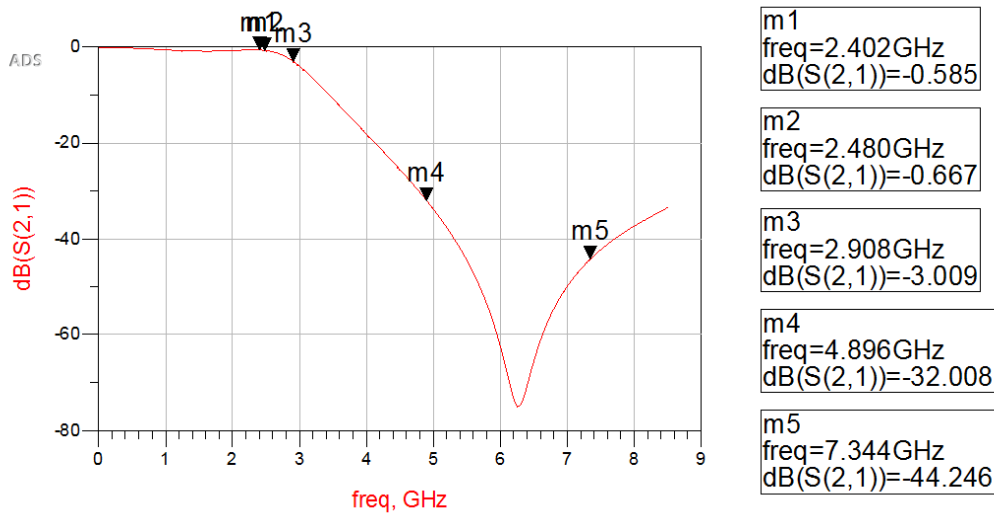


Fig 10. Harmonic frequency rejection filter parameter

As shown in [Fig 10](#), the filter uses two capacitors connected to the ground in parallel and one inductor in series.

The filter's 3-dB corner is at the frequency of 2908 MHz and has a 0.7-dB loss in the range from 2.4 GHz to 2.48 GHz. It has a 32-dB rejection at the second harmonic and a 44-dB rejection at the third harmonic frequency. With a filter with such parameters, the RF performance can pass the RF authentication easily.

8.2 Placement and layout

The component placement and the RF trace layout affect the RF performance.

For the best RF performance, the components must be placed as close as possible to the RF port and the RF trace must be shorted between the RF port and the feed point of the antenna or the SMA connector.

The RF trace must keep a 50-Ω impedance.

The ground at the bottom of the RF components and the RF trace must be complete and solid. No signal trace can go under the RF components and the RF trace.

All the RF components and the RF trace must be on the same layer. No vias are allowed on the RF trace.

The DC-DC components must be placed close to the IDC pin and far away from the RF components and the RF trace.

If using QN9083 in the WLCSP package, make the analog ground separated from the digital ground. It is better to separate the analog ground from the digital ground so that the digital noise does not interfere with the analog parts.

For the WLCSP package, 3G, 1F, 3E, 3F, and 3D are the analog ground pins.

4D, 4C, 5C, 5E, and 5D are the digital pins.

9. Reference design

9.1 QN9080 reference design

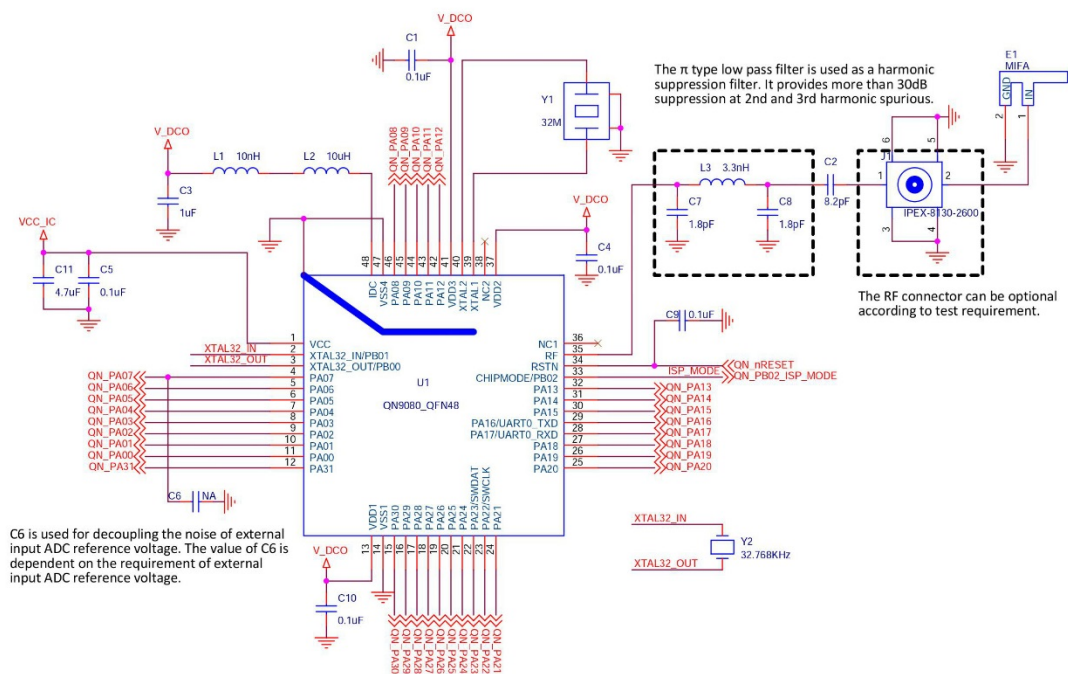


Fig 11. QN9080 with the DC-DC converter reference design schematic

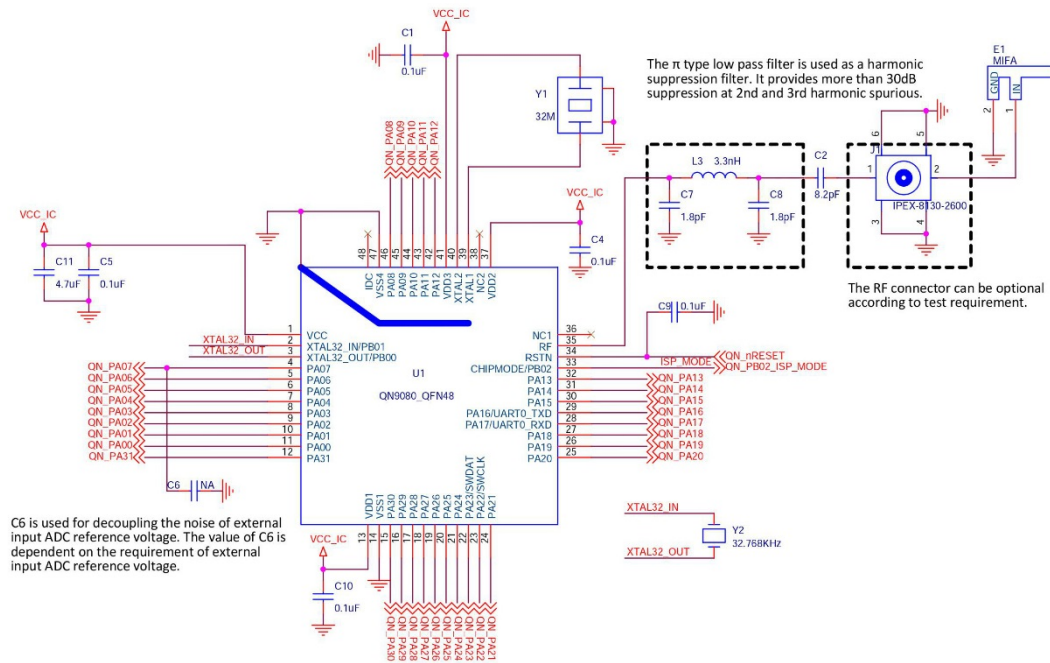


Fig 12. QN9080 without the DC-DC converter reference design schematic

9.2 QN9083 reference design

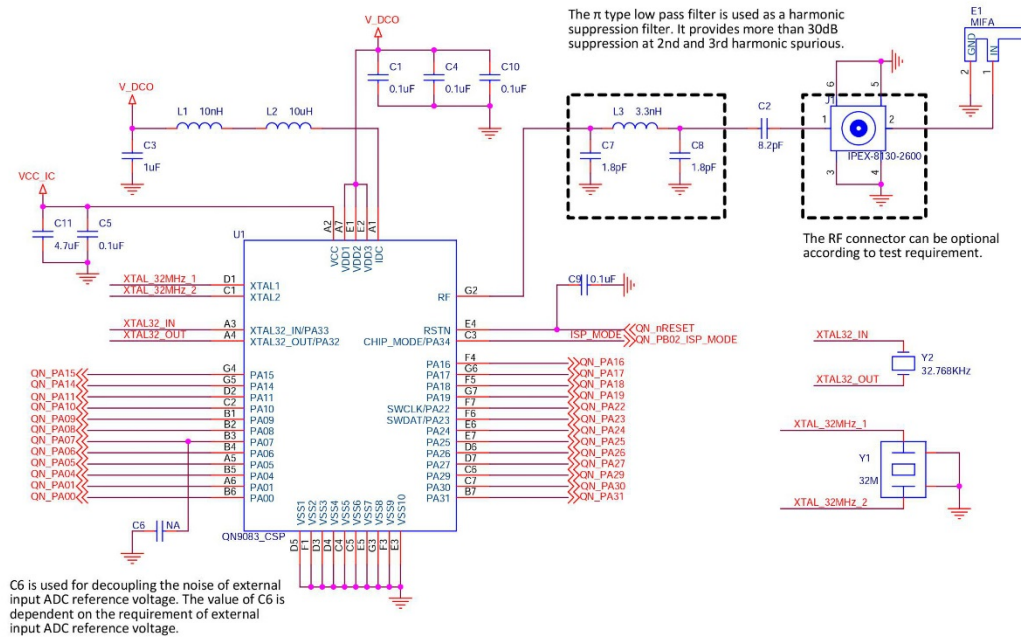


Fig 13. QN9083 with the DC-DC converter reference design schematic

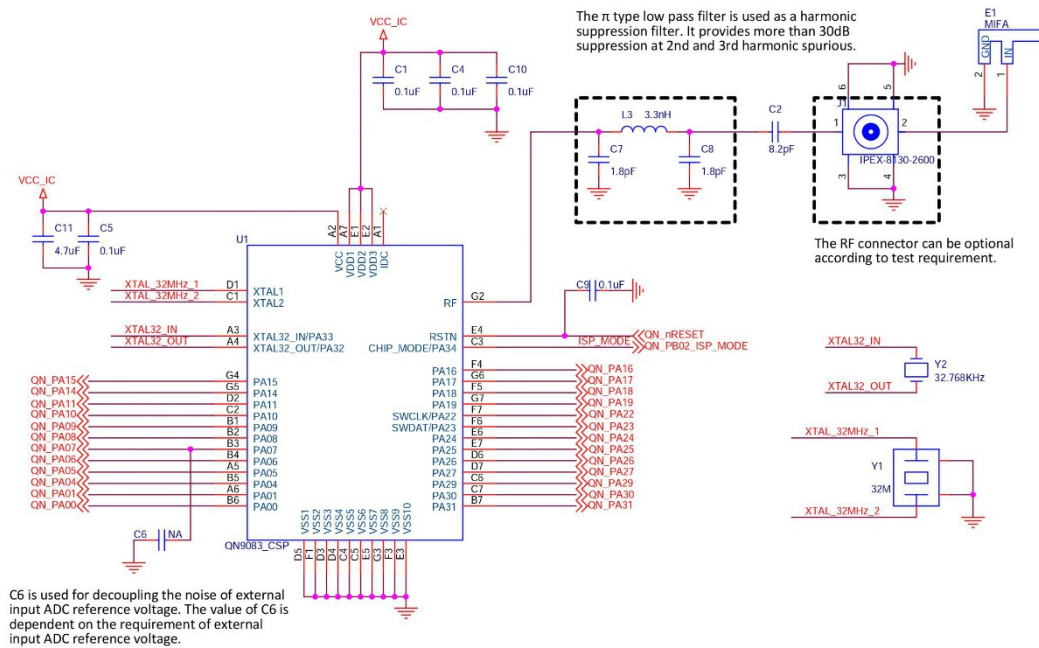


Fig 14. QN9083 without the DC-DC converter reference design schematic

9.3 QN908x minimal BOM design

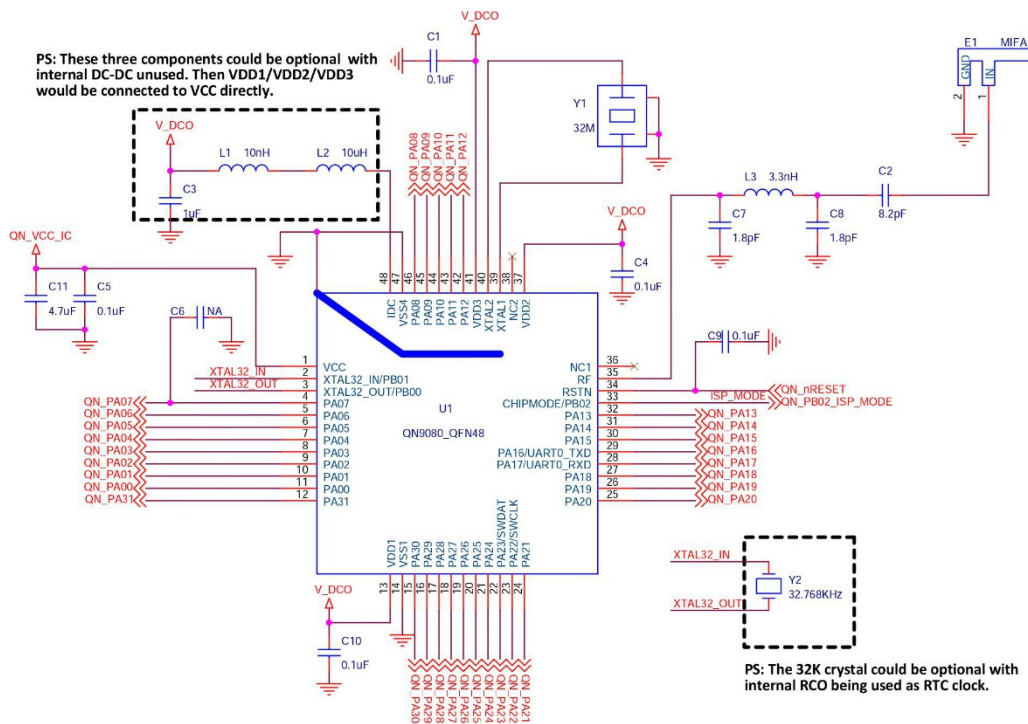


Fig 15. QN908x minimal Bill of Material design schematic

The BOM list of QN908x minimal Bill of Material design is shown in [Table 14](#).

Table 14. QN908x minimal BOM design BOM list

Reference	Part Description	Footprint	MFG	MFG Part Number	Notes
C1, C4, C5, C9, C10	Capacitor, 100 nF, X7R, $\pm 10\%$, 16 V	0402	Murata	GRM155R71C104K A88D	—
C3	Capacitor, 1 μ F, X5R, $\pm 10\%$, 6.3 V	0402	Murata	GRM155R60J105K E19D	Optional ¹
C11	Capacitor, 4.7 μ F, X5R, $\pm 10\%$, 6.3 V	0402	Murata	GRM155R60J475M E47D	—
L2	Inductor, 10 μ H, $\pm 20\%$, 200 mA	0806	Murata	LQH2MCN100M52L	Optional ¹
L2	Inductor, 10 μ H, 20%, 200 mA	0805	TDK	MLZ2012M100WT0 00	Alternative solution ³ Optional ¹
L1	Inductor, 10 μ H, $\pm 5\%$ 0402	0402	Murata	LQG15HN10NJ02D	Optional ¹
Y1	Crystal, 32 MHz, ± 10 ppm, 8 pF, 2.0 x 1.6 x 0.45 mm	2016	Murata	XRCGB32M000F2N 13R0	—
Y1	Crystal, 32 MHz, ± 10 ppm, 8 pF, 2.0 x 1.6 x 0.45 mm	2016	YOKETAN	S2016A-032000-T08-BDD-YNA	Alternative solution ³
Y2	Crystal, 32.768 K, ± 20 ppm, 12.5 pF, 2.05 x 1.2 x 0.6 mm	2012	EPSON	FC-12M-32.7680KA-A5	Optional ²
Y2	Crystal, 32.768 K, ± 20 ppm, 12.5 pF, 2.0 x 1.2 x 0.6 mm	2012	YOKETAN	S2012S-032768-12-20-NA	Optional ²
U1	IC, Bluetooth Low Energy core IC	QFN48	NXP	QN9080	—
C2	Capacitor, 8.2 pF, C0G, ± 0.25 pF, 50 V	0402	Murata	GRM1555C1H8R2C A01D	—
L3	Inductor, 3.3 nH, ± 0.1 nH, 190 mA	0402	Murata	LQP15MN3N3B02	—
C7, C8	Capacitor, 1.8 pF, C0G, ± 0.25 pF, 50 V	0402	Murata	GRM1555C1H1R8C A01D	—
E1	Meandered Inverted-F Antenna	—	—	—	—

1. These components can be optional according to the internal DC/DC converter being used or not.
2. The 32.768-kHz crystal can be optional according to the RTC clock using an internal RCO or an external 32.768-kHz crystal.
3. The alternative solution provides a second solution with a different cost and manufacturer.

10. PCB layout

10.1 PCB stack-up

The recommended PCB stack-up for a QN908x application is shown in [Fig 16](#).

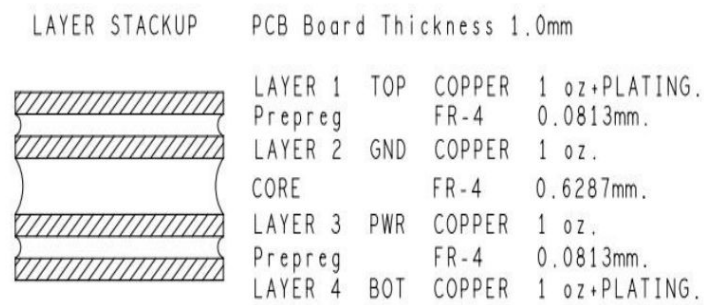


Fig 16. PCB stack-up

The PCB board is 1.0 mm in thickness and based on the standard flame retardant (FR4) material.

10.2 QN9080 PCB layout reference

Top layer

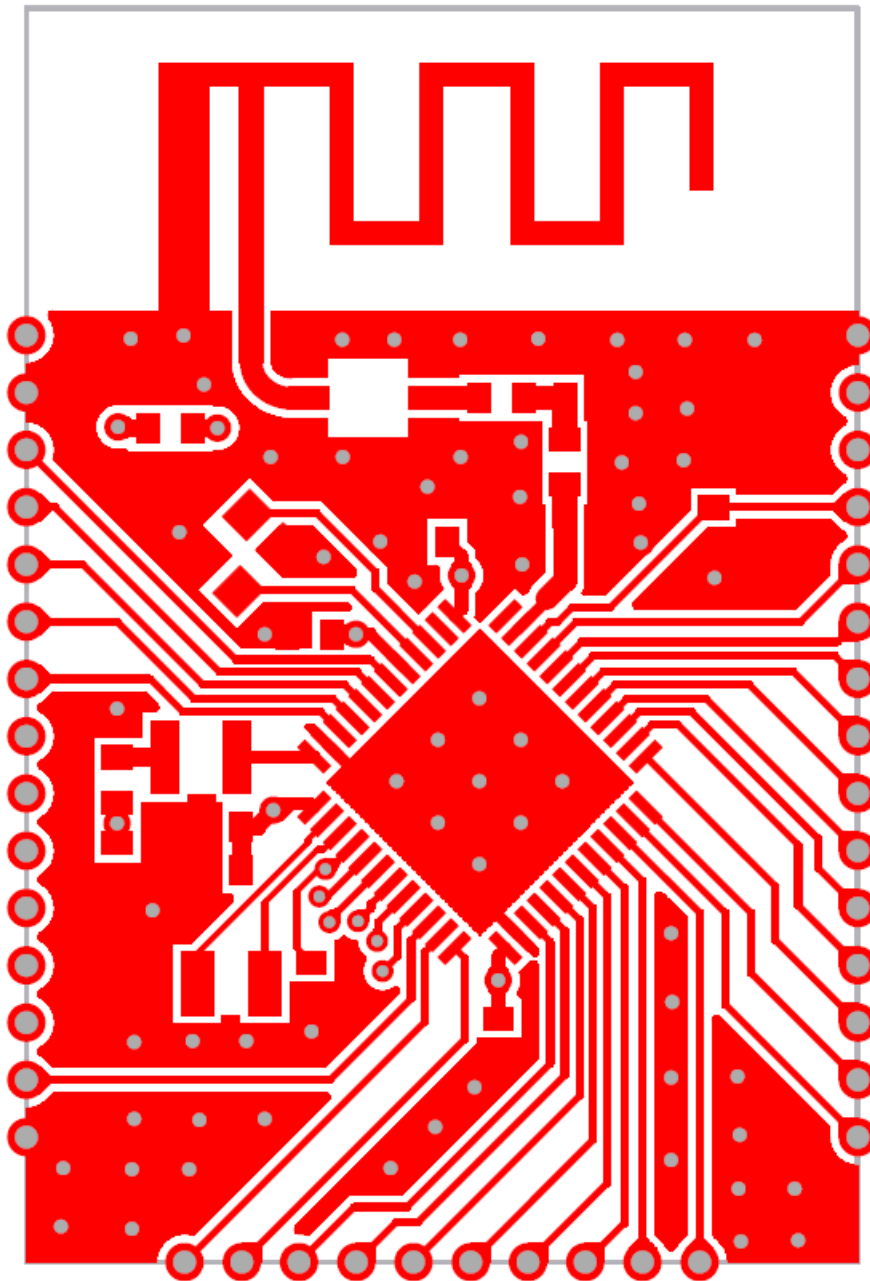


Fig 17. Top layer of the QN9080 PCB layout reference design

GND layer

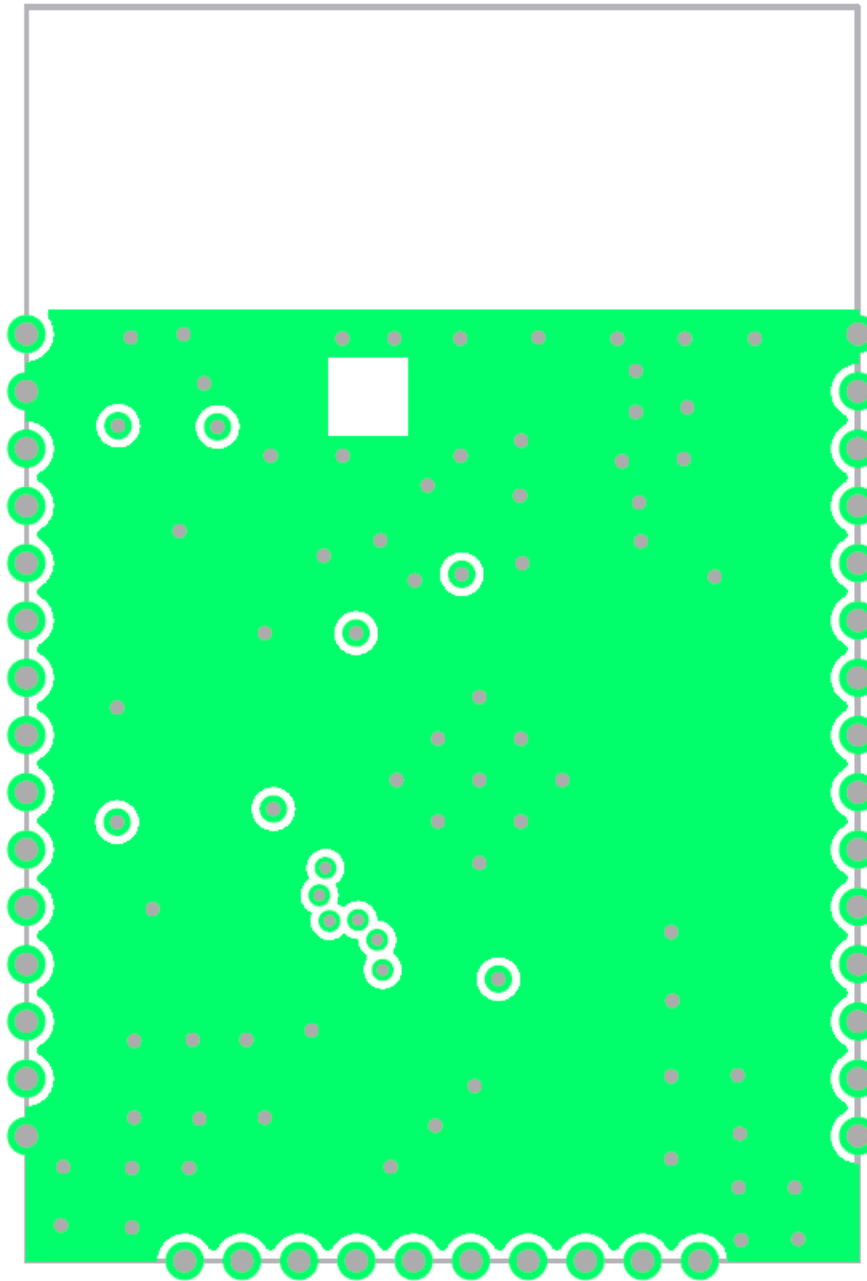


Fig 18. GND layer of the QN9080 PCB layout reference design

Power layer

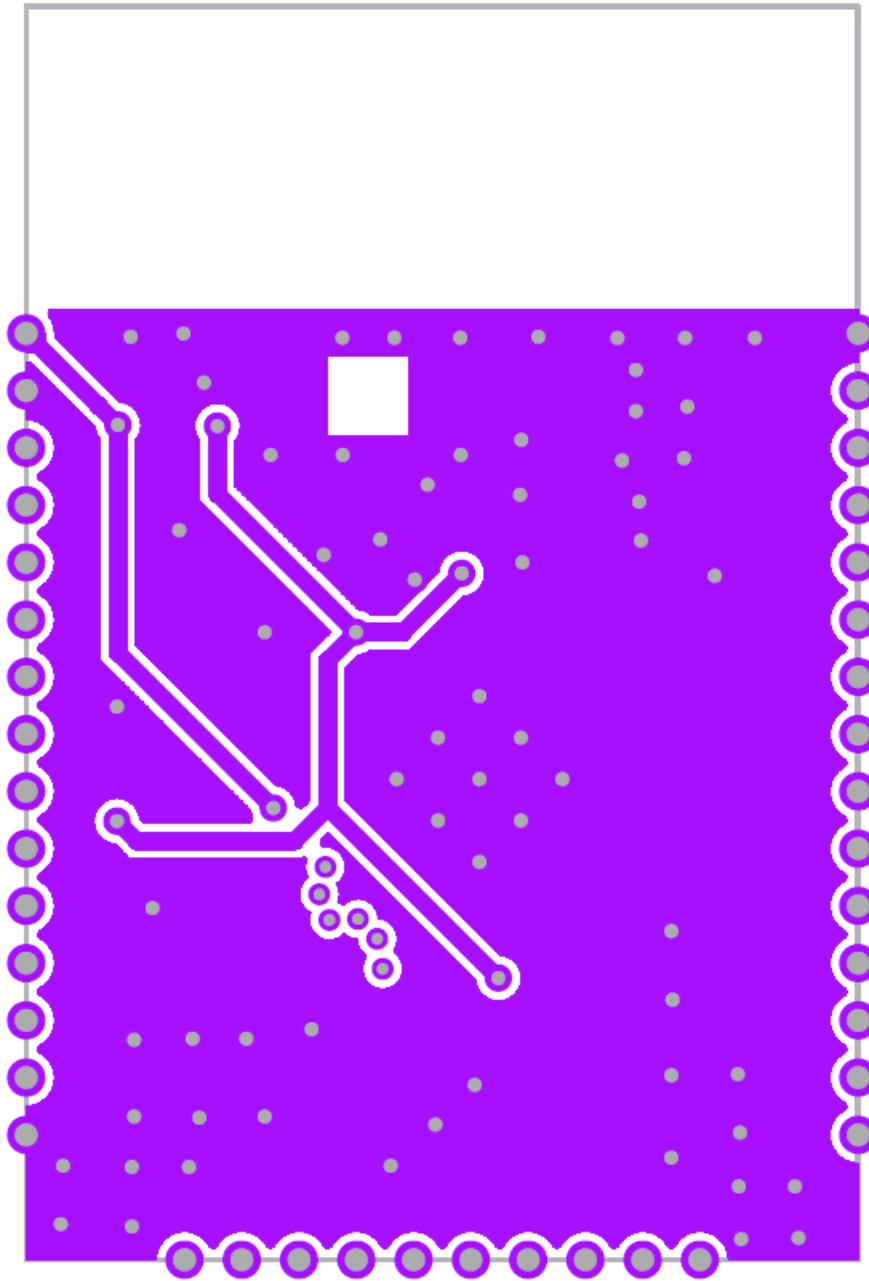


Fig 19. Power layer of the QN9080 PCB layout reference design

Bottom layer

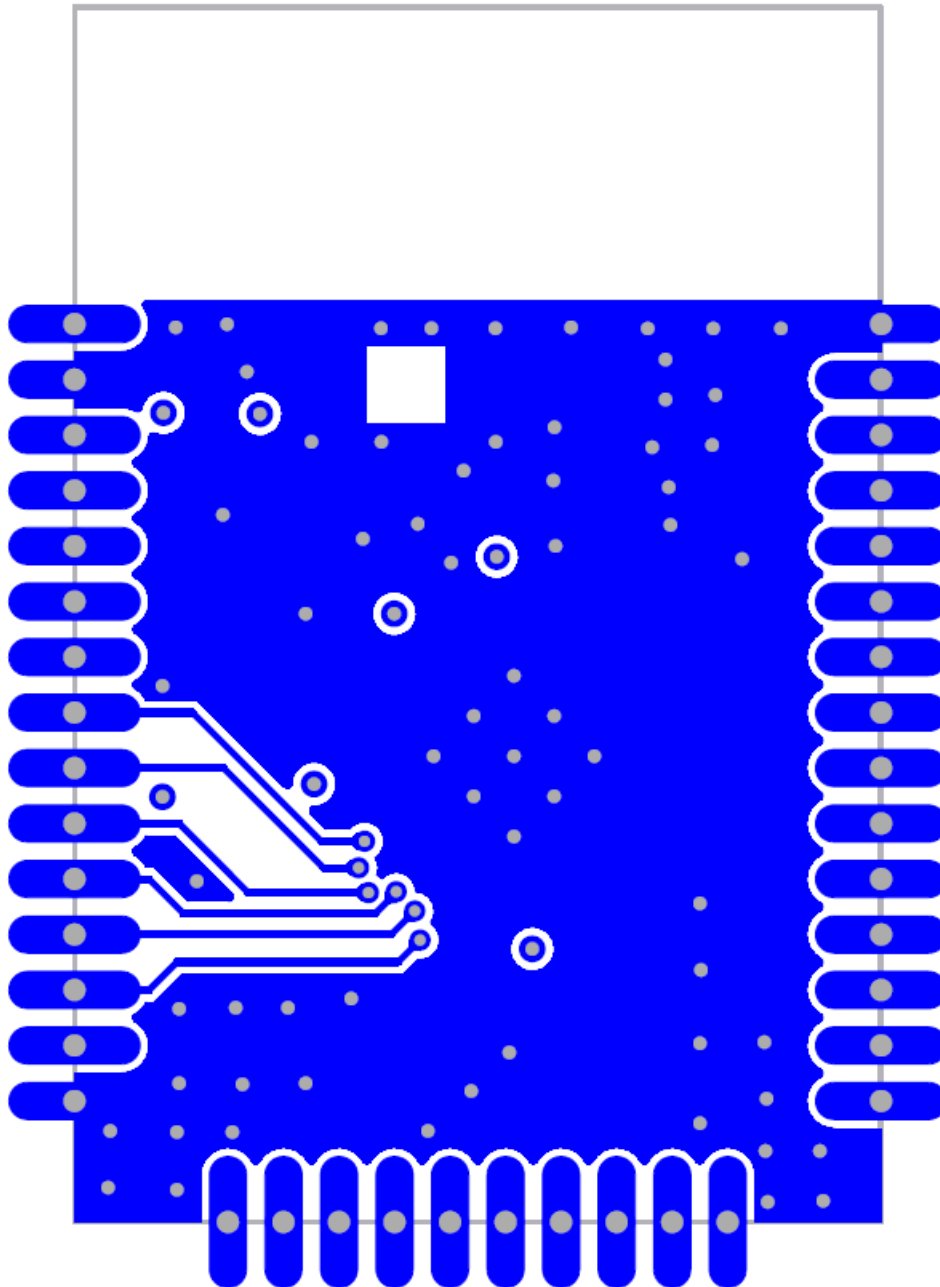


Fig 20. Bottom layer of the QN9080 PCB layout reference design

10.3 QN9083 PCB layout reference

Top layer

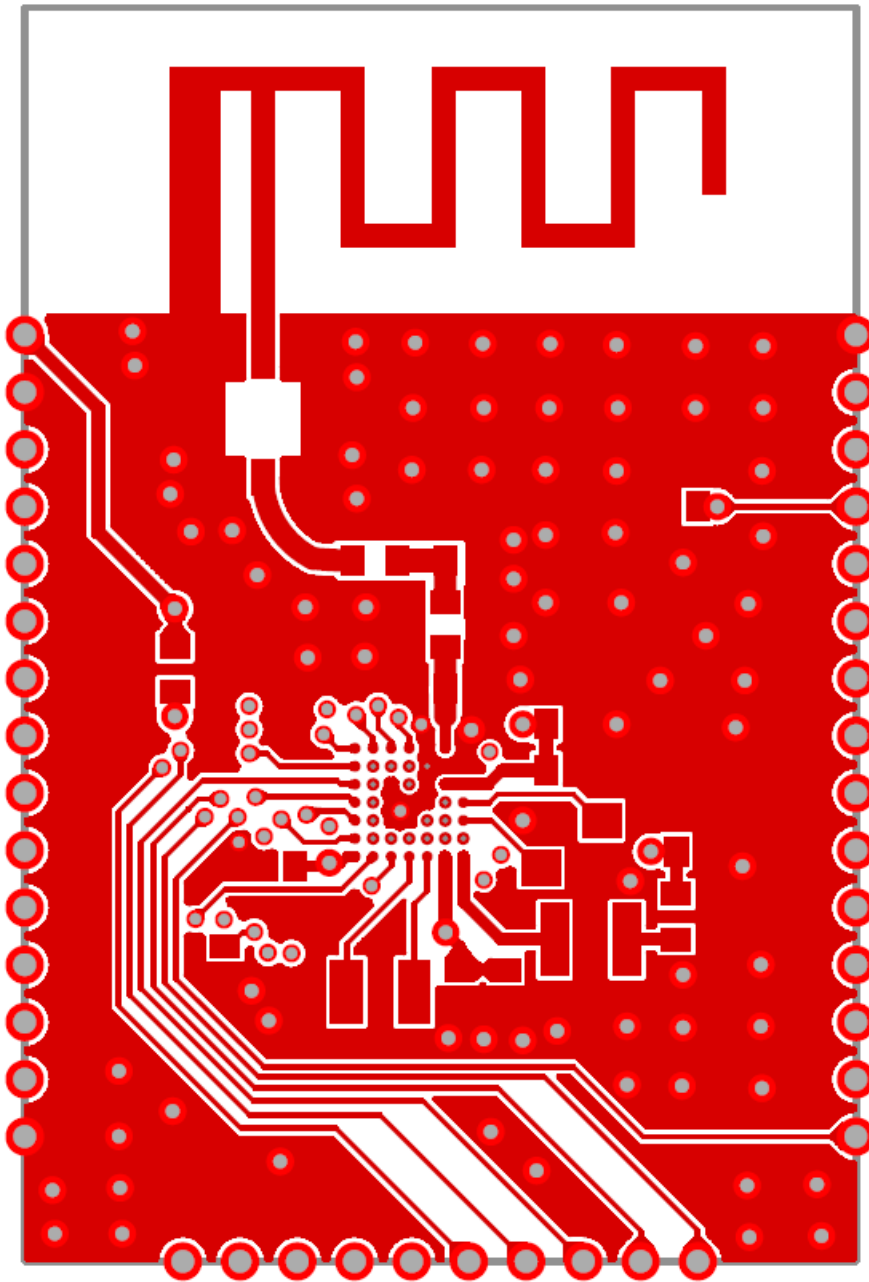


Fig 21. Top layer of the QN9083 PCB layout reference design

GND layer

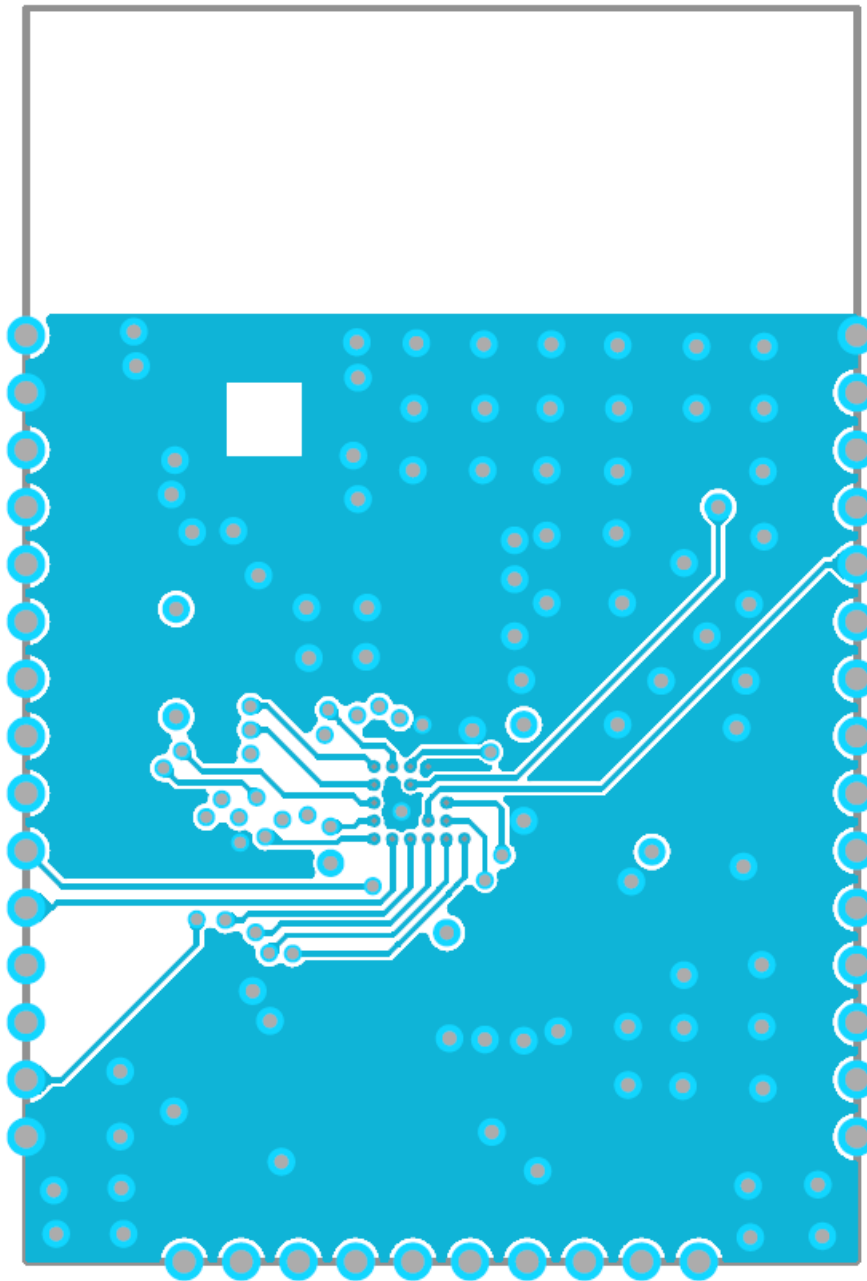


Fig 22. GND layer of the QN9083 PCB layout reference design

Power layer

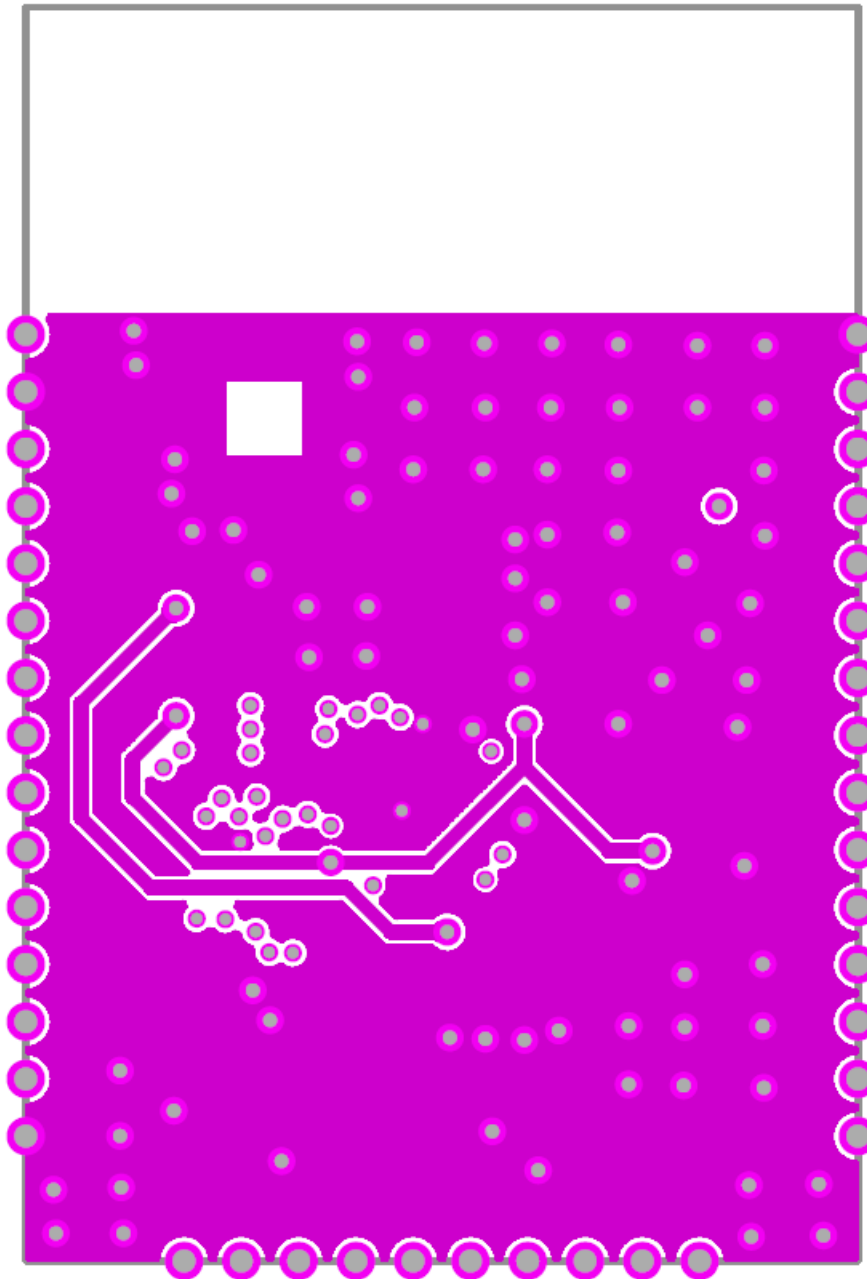


Fig 23. Power layer of the QN9083 PCB layout reference design

Bottom layer

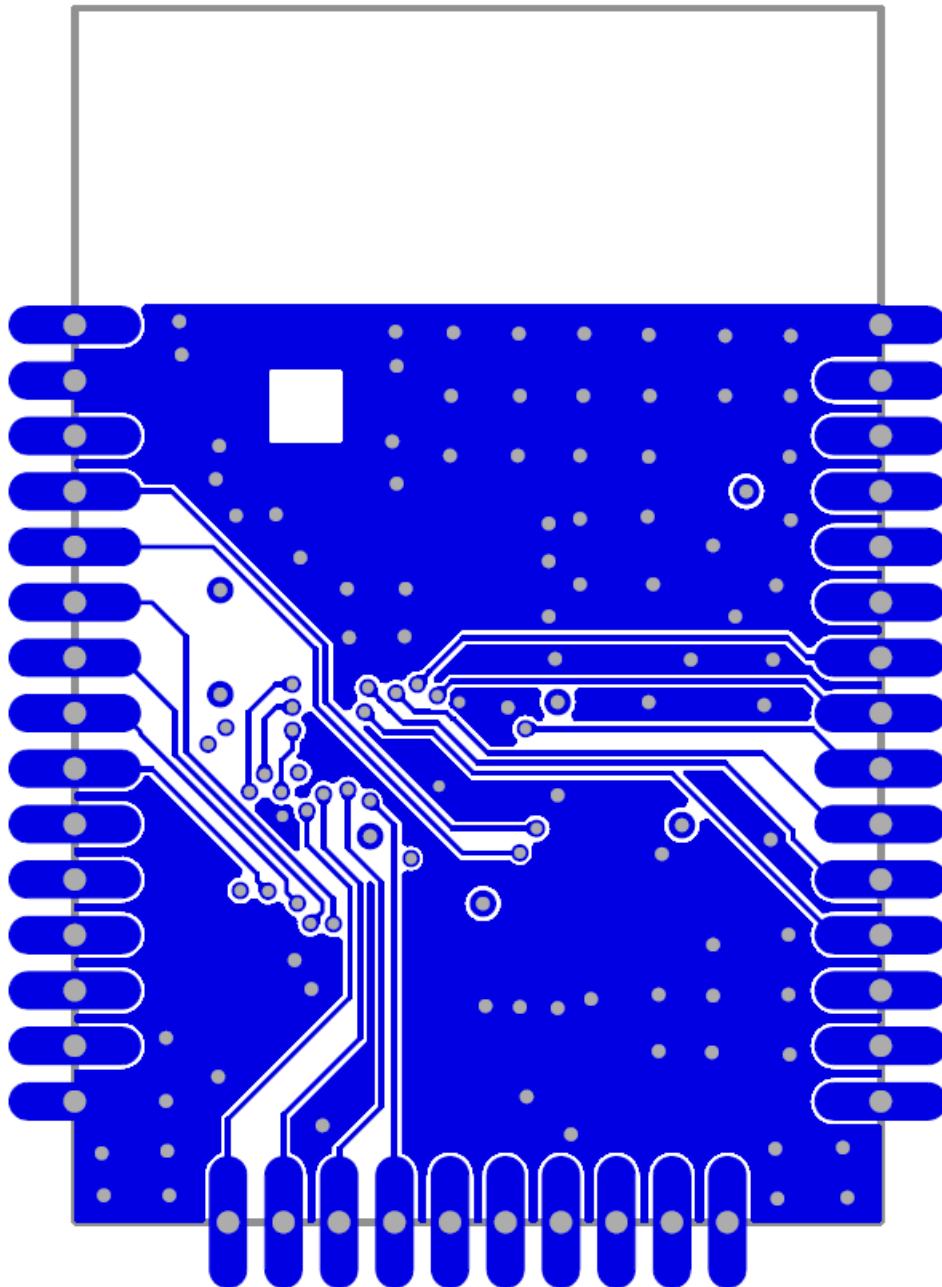


Fig 24. Bottom layer of the QN9083 PCB layout reference design

12. Contents

1.	Introduction	3
2.	System block diagram	3
3.	Pin diagram and pin mux.....	4
3.1	QN9080 HVQFN48 pin diagram.....	4
3.2	QN9080 QFN48 pin mux.....	5
3.3	QN9083 WLCSP pin diagram.....	6
3.4	QN9083 WLCSP pin mux	7
4.	Chip power supply.....	8
4.1	Power supply pins description.....	8
4.2	Integrated DC-DC.....	8
4.3	DC-DC circuit	10
5.	Clock.....	10
5.1	16/32-MHz crystal oscillator (XTAL) and 32-MHz freely running oscillator (OSC32M).....	10
5.2	32.768-kHz crystal oscillator (XTAL32K).....	11
5.3	32-kHz freely running oscillator (RCO32K).....	12
5.4	Clock injection.....	13
5.4.1	Square wave	13
5.4.2	Sine wave.....	13
5.5	Clock output.....	14
6.	IOs.....	14
6.1	Pull-up and pull-down resistors.....	14
6.2	IOs drive strength.....	14
6.2.1	Normal drive ability.....	15
6.2.2	High drive ability.....	15
6.2.3	Extra-high drive ability.....	15
7.	Debug and program.....	15
7.1	Debug port.....	15
7.1.1	SWD.....	15
7.1.2	ETM.....	15
7.2	Programing port.....	15
7.2.1	ISP	15
8.	RF.....	16
8.1	Harmonic rejection.....	16
8.2	Placement and layout.....	17
9.	Reference design.....	18
9.1	QN9080 reference design.....	18
9.2	QN9083 reference design.....	20
9.3	QN908x minimal BOM design.....	22
10.	PCB layout.....	24
10.1	PCB stack-up	24
10.2	QN9080 PCB layout reference.....	25
10.3	QN9083 PCB layout reference.....	29
12.	Contents.....	33
13.	Legal information.....	34
13.1	Definitions.....	34
13.2	Disclaimers.....	34
13.3	Licenses	34
13.4	Patents.....	34
13.5	Trademarks	34

13. Legal information

13.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

13.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. NXP Semiconductors takes no responsibility for the content in this document if provided by an information source outside of NXP Semiconductors.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the *Terms and conditions of commercial sale* of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors and its suppliers accept no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the

customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

Translations — A non-English (translated) version of a document is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

Evaluation products — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out of the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

13.3 Licenses

Purchase of NXP <xxx> components

<License statement text>

13.4 Patents

Notice is herewith given that the subject device uses one or more of the following patents and that each of these patents may have corresponding patents in other jurisdictions.

<Patent ID> — owned by <Company name>

13.5 Trademarks

Notice: All referenced brands, product names, service names and trademarks are property of their respective owners.

<Name> — is a trademark of NXP Semiconductors